

Name of the Student: _____

Question No. 1. Encircle the correct option.**(20)**

- i. A NAND gate gives high output only when
 - a. both inputs are low
 - b. both inputs are high
 - c. both inputs are different
 - d. both inputs are similar
- ii. A transistor can be used as
 - a. diode
 - b. rectifier
 - c. amplifier
 - d. modulator
- iii. The output of transistor used as Common Emitter amplifier is
 - a. positive
 - b. negative
 - c. zero
 - d. very low
- iv. If we decrease I_B then I_C will
 - a. increase
 - b. decrease
 - c. remain constant
 - d. becomes zero
- v. The basic logic gate whose output is '1' when input is '0'
 - a. AND
 - b. OR
 - c. NOT
 - d. NAND
- vi. The output of XOR gate is low when both the inputs are
 - a. high
 - b. low
 - c. similar
 - d. opposite
- vii. Photo diode is used for detection of
 - a. current
 - b. heat
 - c. light
 - d. resistance
- viii. Conversion of A.C. to D.C is called
 - a. amplification
 - b. modulation
 - c. rectification
 - d. oscillation
- ix. When pn junction is reversed biased, the width of depletion region
 - a. increases
 - b. decreases
 - c. remains constant
 - d. becomes infinite
- x. The potential barrier of diode made from silicon is
 - a. 0.7 V
 - b. -0.7 V
 - c. 0.3 V
 - d. 0.5 V
- xi. Collector current in the transistor is greater than base current due to
 - a. large V_{cc}
 - b. large size of collector
 - c. thin base
 - d. all of these
- xii. If $R_1 = \infty$ and $R_2 = 0$, then gain G of a non-inverting operational amplifier is
 - a. -1
 - b. +1
 - c. zero
 - d. infinite
- xiii. The expression for current gain is given by
 - a. $\beta = I_c/I_B$
 - b. $\beta = I_B/I_c$
 - c. $\beta = I_B+I_c$
 - d. $I_c - I_B$
- xiv. LDR is a
 - a. pressure sensor
 - b. photodiode
 - c. light sensor
 - d. it is not a sensor
- xv. The mathematical notation for NAND gate is
 - a. $X=A+B$
 - b. $X=A+B$
 - c. $X=A \cdot B$
 - d. $X = \overline{A \cdot B}$
- xvi. Transistors can be made from
 - a. plastics
 - b. metals
 - c. intrinsic semiconductors
 - d. extrinsic semiconductors
- xvii. The potential barrier in diode stops the movement of
 - a. holes only
 - b. electrons only
 - c. both electrons and holes
 - d. none of these
- xviii. A transistor has a collector current 10 mA and base current 40 μA . Its current gain is
 - a. 400
 - b. 250
 - c. 200
 - d. 125
- xix. The no. of diodes used for full wave rectifier are
 - a. 1
 - b. 2
 - c. 3
 - d. 4
- xx. The photocells are used for
 - a. security system
 - b. counting system
 - c. automatic door system
 - d. all of these

Question No. 2 Write short answers.**2x6=12**

- i. Draw a circuit symbols of n-p-n and p-n-p transistors
- ii. Why ordinary diodes do not emit light?
- iii. What is the net charge on a n-type or a p-type substance?
- iv. What is the effect of forward and reverse biasing of a diode on the width of depletion region?
- v. Why photodiode is operated in reverse biased state?
- vi. What is a potential barrier? Give its value for Si and Ge.
- vii. Give four application of a photodiode.
- viii. What are the biasing requirements for CE transistor as an amplifier?

Q. No. 3 a) Define operational amplifier. Also calculate gain of inverting operational amplifier. **(5)**b) The current flowing into the base of transistor is 100 μA . Find its collector current, its emitter current and ratio of collector current to emitter current if gain of the transistor is 100. **(3)****OR****Q.No. 4 a)** How can be common emitter transistor be used as an amplifier? Calculate its voltage gain. **(5)**b) Calculate the gain of in non-inverting operational amplifier if $R_1 = 10 \text{ k}\Omega$ and $R_2 = 40 \text{ k}\Omega$. **(3)**